

2022/12/12

實驗十二

跳躍指令

姓名：張銀軒 學號：00957050

班級：資工 3A

E-mail：00957050@mail.ntou.edu.tw

注意

1. 繳交時一律轉 PDF 檔
2. 繳交期限為
上完課後
本周日晚上 11:59 前
3. 一人繳交一份
4. 檔名：學號_HW?.pdf
檔名請按照作業檔名格式進行填寫
未依照格式不予批改

2022/12/12

— 、

● 實驗說明：

設計組合語言，用來顯示時鐘的「秒」，運行於 PIC MCU 上。由 00 數到 59 再歸 00，並且不斷重複，將結果輸出於 port_B 上並以 16 進位顯示(10 進位不算分)


請用 BRA 或 BRW 指令代替 GOTO 指令

加分：在課堂實作或補強時將此架構燒錄到 DE0 上的結果給助教檢查，即可加分。兩個七段顯示器分別顯示時鐘的秒之高低位數。接法如圖二


模擬用的組合語言不用加 delay 方便波形觀測

請交 MPLAB 中組合語言截圖、程式碼截圖與波形圖

● 系統硬體架構方塊圖（接線圖）：

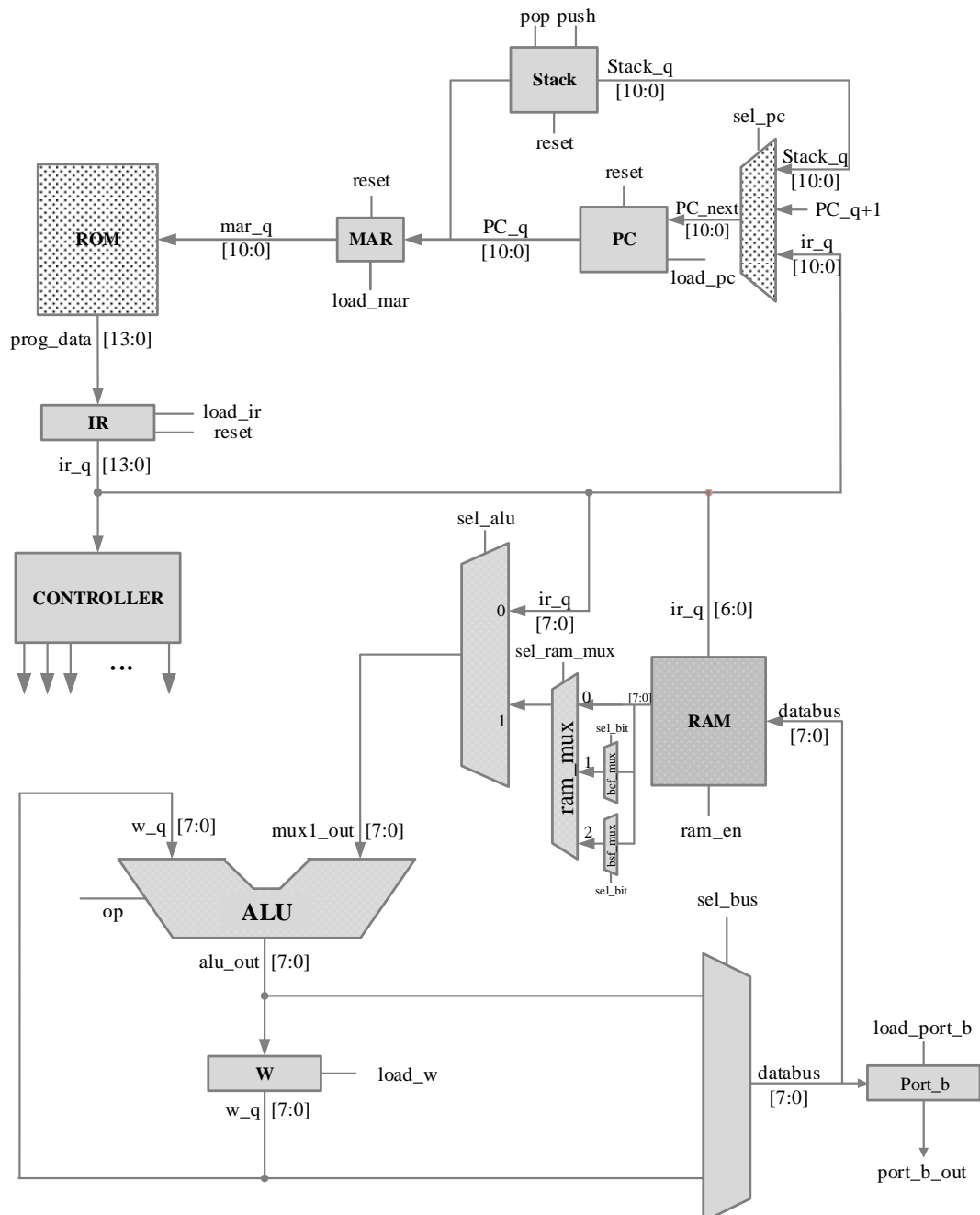

圖一、架構圖

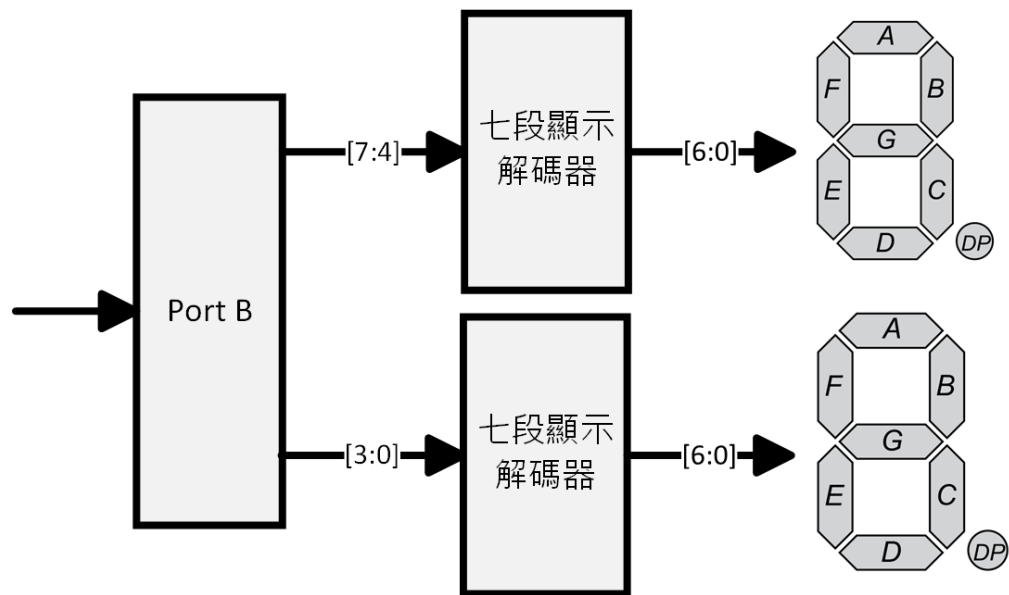

圖二、七段顯示器接法

● 系統架構程式碼、測試資料程式碼與程式碼說明

截圖請善用 win+shift+S

```

C:\...\Program_Rom.asm

temp      equ 0x25
templ     equ 0x24
count1    equ h'20'
count2    equ h'21'
count3    equ h'22'

;Program start
org       0x00      ;reset vector

start     movlw     .60      ; w = 15
          movwf     templ    ; ram[36] = w = 15
          clrf      temp     ; ram[37] <= 0
          clrw      ; w <= 0

loop1     movf      temp,0    ; w = ram[37] = 1
          movwf     PORTB    ; PORTB = w = 1
          movlw     1        ; w <= 1
          addwf     temp,1    ; ram[37] = w+ram[37] = 1+0 = 1
          decfsz    templ,1   ; if(ram[36]-1==0) -> line 23
          bra       loop1
          bra       start
          end
  
```

```

1 module ALU (
2     input [3:0] op,
3     input [7:0] w_q, mux1_out,
4     output logic [7:0] alu_q
5 );
6 always_comb
7 begin
8     case(op)
9         4'h0: alu_q = mux1_out[7:0] + w_q;
10        4'h1: alu_q = mux1_out[7:0] - w_q;
11        4'h2: alu_q = mux1_out[7:0] & w_q;
12        4'h3: alu_q = mux1_out[7:0] | w_q;
13        4'h4: alu_q = mux1_out[7:0] ^ w_q; //XOR
14        4'h5: alu_q = mux1_out[7:0];
15        4'h6: alu_q = mux1_out[7:0] + 1;
16        4'h7: alu_q = mux1_out[7:0] - 1;
17        4'h8: alu_q = 0;
18        4'h9: alu_q = ~mux1_out[7:0];
19        4'hA: alu_q = { mux1_out[7],mux1_out[7:1] }; //ASRF arithmetic right shift
20        4'hB: alu_q = { mux1_out[6:0], 1'b0 }; //LSLF logical left shift
21        4'hC: alu_q = { 1'b0, mux1_out[7:1] }; //LSRF logical right shift
22        4'hD: alu_q = { mux1_out[6:0], mux1_out[7] }; //RLF rotate left f
23        4'hE: alu_q = { mux1_out[0], mux1_out[7:1] }; //RRF rotate right f
24        4'hF: alu_q = { mux1_out[3:0], mux1_out[7:4] }; //{m7, m6,...m4, m3,...m0} => {m3,...m0, m7, m6,...m4}
25        default: alu_q = mux1_out[7:0] + w_q;
26    endcase
27 end
28
29 endmodule

```

```

1 module single_port_ram_128x8(
2     input [7:0]data,
3     input [6:0]addr,
4     input ram_en,
5     input clk,
6     output logic [7:0] ram_out
7 );
8     // Declare the RAM variable
9     //reg [DATA_WIDTH-1:0] ram[2**ADDR_WIDTH-1:0];
10    logic [7:0] ram[127:0];
11
12    always_ff @(posedge clk)
13    begin
14        // Write
15        if (ram_en)
16            ram[addr] <= data;
17    end
18
19    // Continuous assignment implies read returns NEW data.
20    // This is the natural behavior of the TriMatrix memory
21    // blocks in Single Port mode.
22
23    assign ram_out = ram[addr];
24 endmodule

```

```

1 module Program_Rom(
2     output logic [13:0] Rom_data_out,
3     input [10:0] Rom_addr_in
4 );
5
6     logic [13:0] data;
7     always_comb
8     begin
9         case (Rom_addr_in)
10             10'h0 : data = 14'h303C;
11             10'h1 : data = 14'h00A4;
12             10'h2 : data = 14'h01A5;
13             10'h3 : data = 14'h0103;
14             10'h4 : data = 14'h0825;
15             10'h5 : data = 14'h008D;
16             10'h6 : data = 14'h3001;
17             10'h7 : data = 14'h07A5;
18             10'h8 : data = 14'h0BA4;
19             10'h9 : data = 14'h33FA;
20             10'ha : data = 14'h33F5;
21             10'hb : data = 14'h3400;
22             10'hc : data = 14'h3400;
23             default: data = 14'h0;
24         endcase
25     end
26
27     assign Rom_data_out = data;
28
29 endmodule

```

```

1 module sevenSegmentDecoder(
2     output logic [6:0] signal,
3     input [3:0] num
4 );
5     always_comb
6     begin
7         case(num)
8             4'd0 : signal = 7'b100_0000;
9             4'd1 : signal = 7'b111_1001;
10            4'd2 : signal = 7'b010_0100;
11            4'd3 : signal = 7'b011_0000;
12            4'd4 : signal = 7'b001_1001;
13            4'd5 : signal = 7'b001_0010;
14            4'd6 : signal = 7'b000_0010;
15            4'd7 : signal = 7'b111_1000;
16            4'd8 : signal = 7'b000_0000;
17            4'd9 : signal = 7'b001_0000;
18            4'd10 : signal = 7'b000_1000;
19            4'd11 : signal = 7'b000_0011;
20            4'd12 : signal = 7'b100_0110;
21            4'd13 : signal = 7'b010_0001;
22            4'd14 : signal = 7'b000_0110;
23            4'd15 : signal = 7'b000_1110;
24        endcase
25    end
26 endmodule

```

```

1 module Stack (
2     output logic [10:0] stack_out,
3     input [10:0] stack_in,
4     input push,
5     input pop,
6     input reset,
7     input clk
8 );
9     logic [3:0] stk_ptr;
10    logic [10:0] stack [15:0];
11    logic [3:0] stk_index;
12
13    assign stk_index = stk_ptr + 1;
14    assign stack_out = stack[stk_ptr];
15
16    always_ff @( posedge clk ) begin
17        if(reset) begin
18            stk_ptr <= 4'b1111;
19        end
20        else if(push) begin
21            stack[stk_index] <= stack_in;
22            stk_ptr <= stk_ptr + 1;
23        end
24        else if(pop) begin
25            stk_ptr <= stk_ptr - 1 ;
26        end
27    end
28
29 endmodule

```

```

1 module testbench;
2
3     logic clk,reset;
4     logic [7:0] port_b_out;
5
6     cpu cpu_test(
7         .clk(clk),
8         .reset(reset),
9         .port_b_out(port_b_out)
10    );
11
12    always #10 clk = ~clk;
13    initial begin
14        clk = 0; reset = 1;
15        #20 reset = 0;
16        #110000 $stop;
17    end
18 endmodule

```



```

1  module cpu (
2      input clk,
3      input reset,
4      output logic [7:0] port_b_out
5  );
6      logic [13:0] rom_q, ir_q;
7      logic [10:0] pc_next, pc_q, mar_q;
8      logic load_pc, load_mar, load_ir, reset_ir, load_w, ram_en, sel_alu, d, sel_bus;
9      logic load_port_b;
10     logic [1:0] sel_pc;
11     logic [3:0] ps,ns;
12     logic [7:0] w_q, alu_q, ram_out, mux1_out, bcf_mux, bsf_mux, ram_mux;
13     logic [7:0] databus;
14     logic [3:0] op;
15     logic [5:0] opcode;
16     logic [2:0] sel_bit;
17     logic [1:0] sel_ram_mux;
18     //for Stack
19     logic pop, push;
20     logic [10:0] stack_out;
21     //for seven seg
22     logic [6:0] seg0,seg1;
23
24     //Stack
25     Stack Stack_1(
26         .stack_out(stack_out),
27         .stack_in(pc_q),
28         .push(push),
29         .pop(pop),
30         .reset(reset),
31         .clk(clk)
32     );
33
34     assign w_change = {3'b0, w_q};
35     assign k_change = {ir_q[8], ir_q[8], ir_q[8:0]};
36
37     //mux 0 (select next PC address)
38     always_comb begin
39         if(sel_pc == 4) begin
40             pc_next = pc_q + w_change;
41         end
42         else if(sel_pc == 3) begin
43             pc_next = pc_q + k_change;
44         end
45         else if(sel_pc == 2) begin
46             pc_next = stack_out;
47         end
48         else if(sel_pc == 1) begin
49             pc_next = ir_q;
50         end

```

```

51         else begin
52             pc_next = pc_q + 1;
53         end
54     end
55
56     //pc
57     always_ff @( posedge clk ) begin
58         if(reset)
59             pc_q <= 0;
60         else if(load_pc)
61             pc_q <= pc_next;
62     end
63
64     //mar
65     always_ff @( posedge clk ) begin
66         if(load_mar)
67             mar_q <= pc_q;
68     end
69
70     //ROM
71     Program_Rom ROM_1(
72         .Rom_addr_in(mar_q),
73         .Rom_data_out(rom_q)
74     );
75
76     //IR
77     always_ff @( posedge clk ) begin
78         if(reset)
79             ir_q <= 0;
80         else if(load_ir)
81             ir_q <= rom_q;
82     end
83
84     //RAM
85     single_port_ram_128x8 single_port_ram_128x8_1(
86         .data(databus),
87         .addr(ir_q[6:0]),
88         .ram_en(ram_en),
89         .clk(clk),
90         .ram_out(ram_out)
91     );
92
93     assign sel_bit = ir_q[9:7];
94
95     //BCF mux
96     always_comb begin
97         case (sel_bit)
98             3'b000: bcf_mux = ram_out & 8'b1111_1110;
99             3'b001: bcf_mux = ram_out & 8'b1111_1101;
100            3'b010: bcf_mux = ram_out & 8'b1111_1011;

```

```

101         3'b011: bcf_mux = ram_out & 8'b1111_0111;
102         3'b100: bcf_mux = ram_out & 8'b1110_1111;
103         3'b101: bcf_mux = ram_out & 8'b1101_1111;
104         3'b110: bcf_mux = ram_out & 8'b1011_1111;
105         3'b111: bcf_mux = ram_out & 8'b0111_1111;
106     endcase
107 end
108
109 //BSF mux
110 always_comb begin
111     case (sel_bit)
112         3'b000: bsf_mux = ram_out | 8'b0000_0001;
113         3'b001: bsf_mux = ram_out | 8'b0000_0010;
114         3'b010: bsf_mux = ram_out | 8'b0000_0100;
115         3'b011: bsf_mux = ram_out | 8'b0000_1000;
116         3'b100: bsf_mux = ram_out | 8'b0001_0000;
117         3'b101: bsf_mux = ram_out | 8'b0010_0000;
118         3'b110: bsf_mux = ram_out | 8'b0100_0000;
119         3'b111: bsf_mux = ram_out | 8'b1000_0000;
120     endcase
121 end
122
123 //ram mux (select data into mux1)
124 always_comb begin
125     case (sel_ram_mux)
126         0: ram_mux = ram_out;
127         1: ram_mux = bcf_mux;
128         2: ram_mux = bsf_mux;
129     endcase
130 end
131
132 //mux 1 (select data into ALU)
133 always_comb begin
134     if(sel_alu) begin
135         mux1_out = ram_mux;
136     end
137     else begin
138         mux1_out = ir_q;
139     end
140 end
141
142 assign d = ir_q[7];
143 assign MOVLW = (ir_q[13:8]==6'h30);
144 assign ADDLW = (ir_q[13:8]==6'h3E);
145 assign IORLW = (ir_q[13:8]==6'h38);
146 assign ANDLW = (ir_q[13:8]==6'h39);
147 assign SUBLW = (ir_q[13:8]==6'h3C);
148 assign XORLW = (ir_q[13:8]==6'h3A);
149
150 assign ADDWF = (ir_q[13:8]==6'h07);

```



```

151 assign ANDWF = (ir_q[13:8]==6'h05);
152 assign CLRf = (ir_q[13:8]==6'h01 && d==1);
153 assign CLRW = (ir_q[13:4]==10'h010 && ir_q[3:2]==2'h0);
154 assign COMf = (ir_q[13:8]==6'h09);
155 assign DECF = (ir_q[13:8]==6'h03);
156 assign GOTO = (ir_q[13:11]==3'b101);
157
158 assign INCF = (ir_q[13:8]==6'h0A);
159 assign IORWF = (ir_q[13:8]==6'h04);
160 assign MOVf = (ir_q[13:8]==6'h08);
161 assign MOVWF = (ir_q[13:8]==6'h00 && ir_q[7]==1'b1);
162 assign SUBWF = (ir_q[13:8]==6'h02);
163 assign XORWF = (ir_q[13:8]==6'h06);
164
165 assign BCF = (ir_q[13:12]==2'b01 && ir_q[11:10]==2'b00);
166 assign BSF = (ir_q[13:12]==2'b01 && ir_q[11:10]==2'b01);
167 assign BTFSC = (ir_q[13:12]==2'b01 && ir_q[11:10]==2'b10);
168 assign BTFSS = (ir_q[13:12]==2'b01 && ir_q[11:10]==2'b11);
169 assign DECFSZ = (ir_q[13:8]==6'h0B);
170 assign INCFSZ = (ir_q[13:8]==6'h0F);
171
172 assign btfsc_skip_bit = (ram_out[ir_q[9:7]]==0);
173 assign btfss_skip_bit = (ram_out[ir_q[9:7]]==1);
174 assign btfsc_btfss_skip_bit = (BTFSC&btfsc_skip_bit) |
175                               (BTFSS&btfss_skip_bit);
176 assign ASRF = (ir_q[13:8]==6'h37); // arithmetic right shift
177 assign LSLF = (ir_q[13:8]==6'h35); // logical left shift
178 assign LSRF = (ir_q[13:8]==6'h36); // logical right shift
179 assign RLF = (ir_q[13:8]==6'h0D); // rotate left f
180 assign RRF = (ir_q[13:8]==6'h0C); // rotate right f
181 assign SWAP = (ir_q[13:8]==6'h0E); //{m7, m6,...m4, m3,...m0} => {m3,...m0, m7, m6,...m4}
182
183 assign CALL = (ir_q[13:12]==2'b10 && ir_q[11]==0);
184 assign RETURN = (ir_q == 0);
185
186 assign BRA = (ir_q[13:12]==2'b11 && ir_q[11:9]==3'b001); // relative branch
187 assign BRW = (ir_q[13:0]==6'h000B); // relative branch with W
188 assign NOP = (ir_q[13:0]==6'h000B); // no operation
189
190 //ALU
191 ALU ALU_1(
192     .op(op),
193     .w_q(w_q),
194     .mux1_out(mux1_out),
195     .alu_q(alu_q)
196 );
197 assign aluout_zero = (alu_q == 0);
198
199 //register
200 always_ff @( posedge clk ) begin

```

```

201         if(load_w)
202             w_q <= alu_q;
203         end
204
205         //mux 2 (select data into RAM)
206         always_comb begin
207             if(sel_bus) begin
208                 databus = w_q;
209             end
210             else begin
211                 databus = alu_q;
212             end
213         end
214
215         //Port_b
216         always_ff @( posedge clk ) begin
217             if(reset) begin
218                 port_b_out <= 0;
219             end
220             else if(load_port_b) begin
221                 port_b_out <= databus;
222             end
223         end
224
225         logic [3:0] ten,unit;
226         always_comb begin
227             ten = port_b_out / 10;
228             unit = port_b_out - ten * 10;
229         end
230         //seven seg 0
231         sevenSegmentDecoder sevenSegmentDecoder_0(
232             .signal(seg0),
233             .num(ten)
234         );
235
236         //seven seg 1
237         sevenSegmentDecoder sevenSegmentDecoder_1(
238             .signal(seg1),
239             .num(unit)
240         );
241
242         assign addr_port_b = (ir_q[6:0] == 7'h0D);
243
244         //controller
245         parameter T0 = 0;
246         parameter T1 = 1;
247         parameter T2 = 2;
248         parameter T3 = 3;
249         parameter T4 = 4;
250         parameter T5 = 5;

```

```

251     parameter T6 = 6;
252
253     always_ff @( posedge clk ) begin
254         if(reset) ps <= 0;
255         else ps <= ns;
256     end
257
258     always_comb begin
259         sel_alu = 0;
260         sel_pc = 0;
261         load_mar = 0;
262         load_pc = 0;
263         reset_ir = 1;
264         load_ir = 0;
265         load_w = 0;
266         ram_en = 0;
267         op =0;
268         sel_ram_mux = 0;
269         sel_bus = 0;
270         load_port_b = 0;
271         ns=0;
272         //for Stack
273         push = 0;
274         pop = 0;
275         case(ps)
276             T0: begin
277                 ns = T1;
278             end
279             T1: begin
280                 load_mar = 1;
281                 load_pc = 0;
282                 reset_ir = 0;
283                 load_ir = 0;
284                 load_w = 0;
285                 ns = T2;
286             end
287             T2: begin
288                 sel_pc = 0;
289                 load_mar = 0;
290                 load_pc = 1;
291                 reset_ir = 0;
292                 load_ir = 0;
293                 load_w = 0;
294                 ns = T3;
295             end
296             T3: begin
297                 load_mar = 0;
298                 load_pc = 0;
299                 reset_ir = 0;
300                 load_ir = 1;

```

```
301         load_w = 0;
302         ns = T4;
303     end
304     T4: begin
305         load_mar = 0;
306         load_pc = 0;
307         reset_ir = 0;
308         load_ir = 0;
309
310         if(MOVLW) begin
311             sel_alu = 0;
312             op = 5;
313             load_w = 1;
314         end
315         else if(ADDLW) begin
316             sel_alu = 0;
317             op = 0;
318             load_w = 1;
319         end
320         else if(IORLW) begin
321             sel_alu = 0;
322             op = 3;
323             load_w = 1;
324         end
325         else if(ANDLW) begin
326             sel_alu = 0;
327             op = 2;
328             load_w = 1;
329         end
330         else if(SUBLW) begin
331             sel_alu = 0;
332             op = 1;
333             load_w = 1;
```

```
334 end
335 else if(XORLW) begin
336     sel_alu = 0;
337     op = 4;
338     load_w = 1;
339 end
340
341
342 else if(GOTO) begin
343     sel_pc = 1;
344     load_pc = 1;
345 end
346 else if(ADDWF) begin
347     op = 0;
348     sel_alu = 1;
349     if(d) begin
350         ram_en = 1;
351     end
352     else begin
353         load_w = 1;
354     end
355 end
356 else if(ANDWF) begin
357     op = 2;
358     sel_alu = 1;
359     if(d) begin
360         ram_en = 1;
361     end
362     else begin
363         load_w = 1;
364     end
365 end
366 else if(CLRF) begin
```

```
367         op = 8;
368         ram_en = 1;
369     end
370     else if(CLRW) begin
371         op = 8;
372         load_w = 1;
373     end
374     else if(COMF) begin
375         op = 9;
376         sel_alu = 1;
377         ram_en = 1;
378     end
379     else if(DECF) begin
380         op = 7;
381         sel_alu = 1;
382         ram_en = 1;
383     end
384
385     else if(INCF) begin
386         op = 6;
387         sel_alu = 1;
388         if(d) begin
389             ram_en = 1;
390             sel_bus = 0;
391         end
392         else begin
393             load_w = 1;
394         end
395     end
396     else if(IORWF) begin
397         op = 3;
398         sel_alu = 1;
399         if(d) begin
400             ram_en = 1;
```



```
401         sel_bus = 0;
402     end
403     else begin
404         load_w = 1;
405     end
406 end
407 else if(MOVF) begin
408     op = 5;
409     sel_alu = 1;
410     if(d) begin
411         ram_en = 1;
412         sel_bus = 0;
413     end
414     else begin
415         load_w = 1;
416     end
417 end
418 else if(MOVWF) begin
419     sel_bus = 1;
420     if(addr_port_b)begin
421         load_port_b = 1;
422     end
423     else begin
424         ram_en = 1;
425     end
426 end
427 else if(SUBWF) begin
428     op = 1;
429     sel_alu = 1;
430     if(d) begin
431         ram_en = 1;
432         sel_bus = 0;
433     end
```

```
434         else begin
435             load_w = 1;
436         end
437     end
438     else if(XORWF) begin
439         op = 4;
440         sel_alu = 1;
441         if(d) begin
442             ram_en = 1;
443             sel_bus = 0;
444         end
445         else begin
446             load_w = 1;
447         end
448     end
449     else if(BCF)begin
450         sel_alu = 1;
451         sel_ram_mux = 1;
452         op = 5;
453         sel_bus = 0;
454         ram_en = 1;
455     end
456     else if(BSF)begin
457         sel_alu = 1;
458         sel_ram_mux = 2;
459         op = 5;
460         sel_bus = 0;
461         ram_en = 1;
462     end
463     else if(BTFSC || BTFSS)begin
464         if( btfsc_btfss_skip_bit )begin
465             load_pc = 1;
466             sel_pc = 0;
```

```
467         end
468     end
469     else if(DECFSZ)begin
470         sel_alu = 1;
471         op = 7;
472         if(aluout_zero)begin
473             load_pc = 1;
474             sel_pc = 0;
475         end
476
477         if(d)begin
478             ram_en = 1;
479             sel_bus = 0;
480         end
481         else begin
482             load_w = 1;
483         end
484     end
485     else if(INCFSZ) begin
486         sel_alu = 1;
487         op = 6;
488         if(aluout_zero)begin
489             load_pc = 1;
490             sel_pc = 0;
491         end
492
493         if(d)begin
494             ram_en = 1;
495             sel_bus = 0;
496         end
497         else begin
498             load_w = 1;
499         end
500     end
```

```
501
502     else if(ASRF) begin
503         sel_alu = 1;
504         sel_ram_mux = 0;
505         op = 4'hA;
506         if(d)begin
507             sel_bus = 0;
508             ram_en = 1;
509         end
510         else begin
511             load_w = 1;
512         end
513     end
514     else if(LSLF) begin
515         sel_alu = 1;
516         sel_ram_mux = 0;
517         op = 4'hB;
518         if(d)begin
519             sel_bus = 0;
520             ram_en = 1;
521         end
522         else begin
523             load_w = 1;
524         end
525     end
526     else if(LSRF) begin
527         sel_alu = 1;
528         sel_ram_mux = 0;
529         op = 4'hC;
530         if(d)begin
531             sel_bus = 0;
532             ram_en = 1;
533         end
```


```
534         else begin
535             load_w = 1;
536         end
537     end
538     else if(RLF) begin
539         sel_alu = 1;
540         sel_ram_mux = 0;
541         op = 4'hD;
542         if(d)begin
543             sel_bus = 0;
544             ram_en = 1;
545         end
546         else begin
547             load_w = 1;
548         end
549     end
550     else if(RRF) begin
551         sel_alu = 1;
552         sel_ram_mux = 0;
553         op = 4'hE;
554         if(d)begin
555             sel_bus = 0;
556             ram_en = 1;
557         end
558         else begin
559             load_w = 1;
560         end
561     end
562     else if(SWAP) begin
563         sel_alu = 1;
564         sel_ram_mux = 0;
565         op = 4'hF;
566         if(d)begin
```

```

567         sel_bus = 0;
568         ram_en = 1;
569     end
570     else begin
571         load_w = 1;
572     end
573 end
574
575     else if(CALL) begin
576         sel_pc = 1;
577         load_pc = 1;
578         push = 1;
579     end
580     else if(RETURN) begin
581         sel_pc = 2;
582         load_pc = 1;
583         pop = 1;
584     end
585     else if(BRW) begin
586         load_pc = 1;
587         sel_pc = 4;
588     end
589     else if(BRA) begin
590         load_pc = 1;
591         sel_pc = 3;
592     end
593     ns = T5;
594 end
595 T5: begin
596     ns = T6;
597 end
598 T6: begin
599     ns = T1;
600 end
601 endcase
602 end
603 endmodule

```

● 模擬結果與結果說明：

 

1. 能從 0 數到 59，接著再從 0 開始，一直循環
2. 能依照當下的數字輸出十位數字和個位數字的 7 段顯示器訊號

二、


● 實驗說明：

用 MPLAB 設計一個 Rom，使 0x21 和 0x22 兩個位址的 16 進制(用 10 進位顯示不算分)分別表示時鐘的分及秒，即 0x22(秒)的 16 進制會由 1 數到 59 後歸零，每當 0x22(秒)歸零 0x21(分)就會加 1

模擬用的組合語言不用加 delay 方便波形觀測

請交 MPLAB 中組合語言截圖、程式碼截圖與波形圖，存分跟秒的暫存器請分別設定為 0x21 跟 0x22

● 系統硬體架構方塊圖（接線圖）：

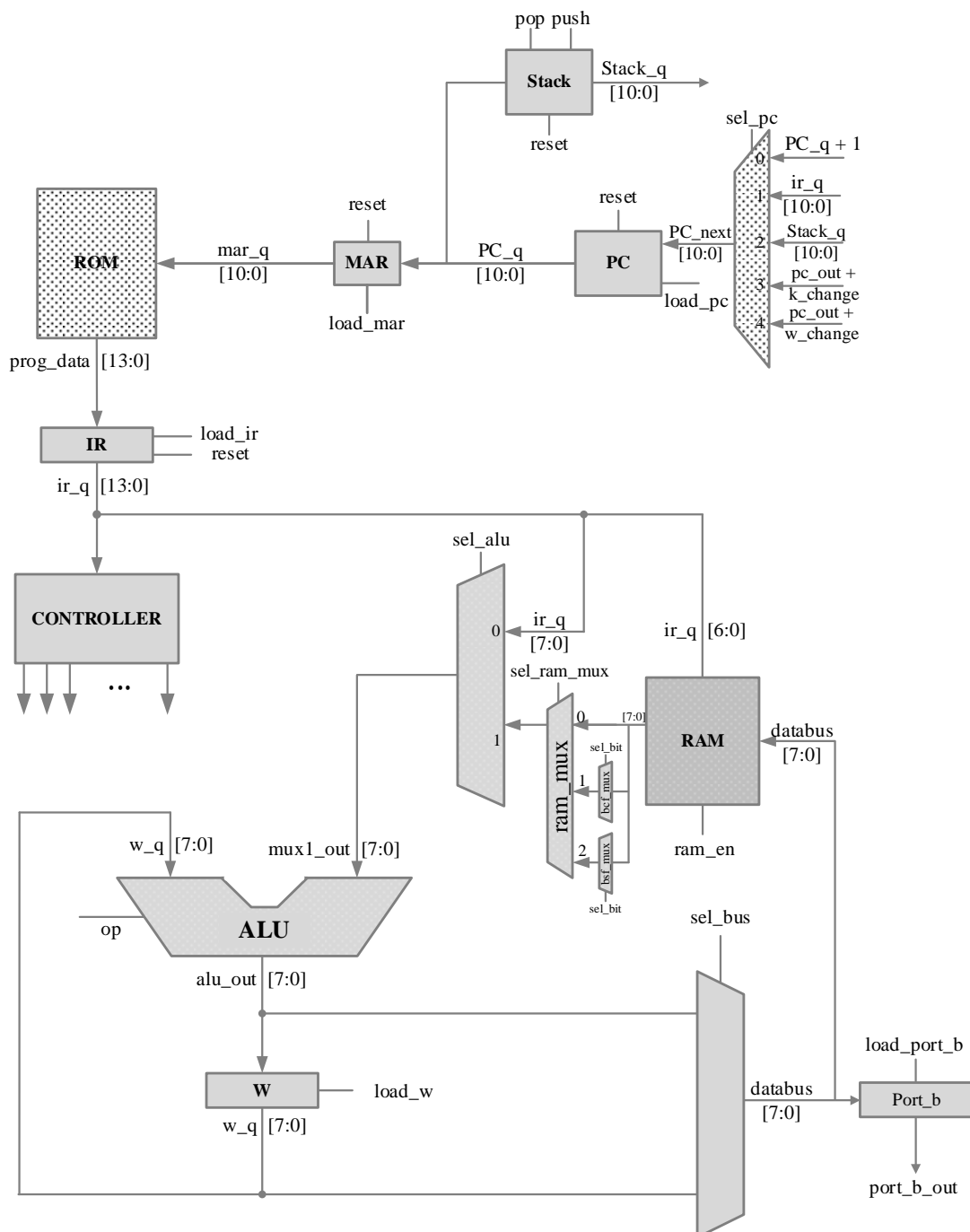

架構圖

- 系統架構程式碼、測試資料程式碼與程式碼說明
截圖請善用 win+shift+S

- 模擬結果與結果說明：

● 結論與心得：

