

2022/11/14

實驗八

暫存器定址

姓名：張銀軒 學號：00957050

班級：資工 3A

E-mail：00957050@mail.ntou.edu.tw

注意


1. 繳交時一律轉 PDF 檔
2. 繳交期限為
上完課後
當週五晚上 12 點前
3. 一人繳交一份
4. 檔名：學號_HW?.pdf
檔名請按照作業檔名格式進行填寫
未依照格式不予批改

● 實驗說明：

1. 如圖所示，設計一個架構實現暫存器定址的指令
2. 輸入：clk, reset
3. 輸出：w_q[7:0]

下方有附 Rom 的截圖，請務必按照規定的 input 及 output 來做

● 系統硬體架構方塊圖（接線圖）：

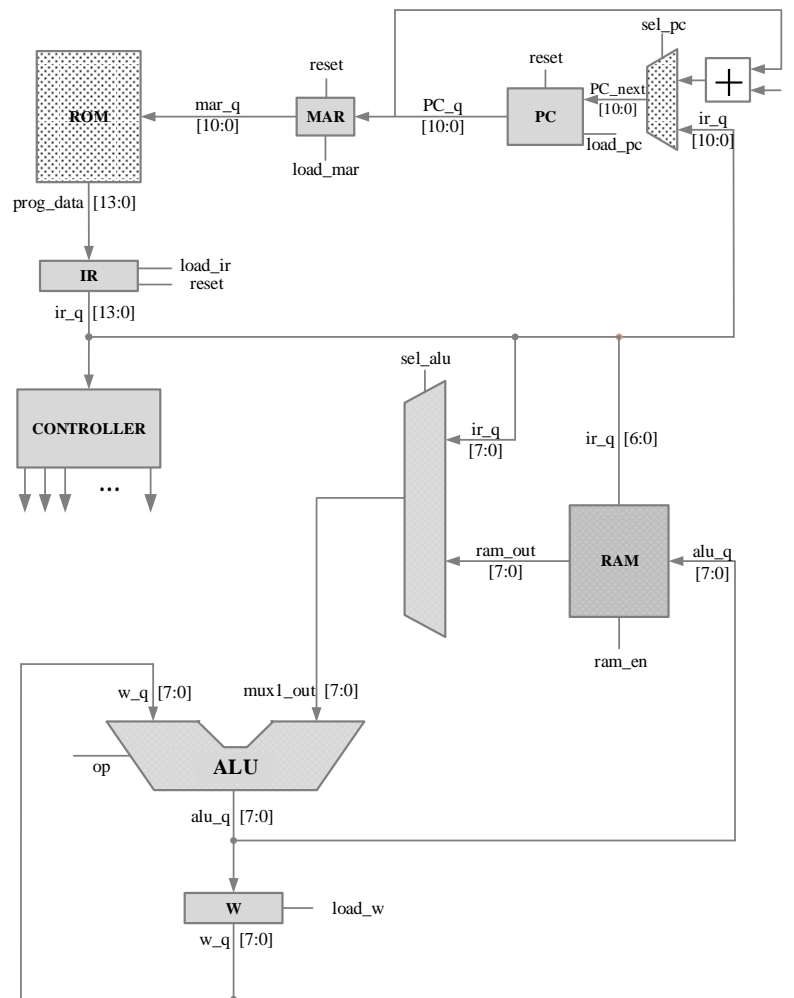

架構圖

```

module Program_Rom(
    output logic [13:0] Rom_data_out,
    input [10:0] Rom_addr_in
);
//-----
    logic [13:0] data;

    always_comb
    begin
        case (Rom_addr_in)
            11'h0: data = 14'h01A5; //CLRF      ram[25]=0
            11'h1: data = 14'h0103; //CLRWF   w=0
            11'h2: data = 14'h3006; //MOVLW 6   w=6
            11'h3: data = 14'h07A5; //ADDLW 0x25,1 ram[25]=6
            11'h4: data = 14'h3005; //MOVLW 5   w=5
            11'h5: data = 14'h0725; //ADDWF 0x25,0 w=11
            11'h6: data = 14'h3E02; //ADDLW 2   w=13
            11'h7: data = 14'h05A5; //ANDWF 0x25,1 ram[25]=4
            11'h8: data = 14'h03A5; //DECF 0x25   ram[25]=3
            11'h9: data = 14'h09A5; //COMF 0x25   ram[25]=252
            11'ha: data = 14'h280A; //GOTO 8
            //這兩行為MPLAB清除暫存器的指令，不用管
            11'hb: data = 14'h3400;
            11'hc: data = 14'h3400;
            default: data = 14'h0;
        endcase
    end
    assign Rom_data_out = data;
endmodule

```

Program_Rom

● 系統架構程式碼、測試資料程式碼與程式碼說明(.sv 檔及.do 檔都要截圖)

截圖請善用 win+shift+S

```
1 module Program_Rom (//1114 class lesson
2     output logic [13:0] Rom_data_out,
3     input [10:0] Rom_addr_in
4 );
5     logic [13:0] data;
6     always_comb begin
7         case (Rom_addr_in)
8             11'h0: data = 14'h01A5; //CLRF          ram[25]=0
9             11'h1: data = 14'h0103; //CLRW          w=0
10            11'h2: data = 14'h3006; //MOVLW 6        w=6
11            11'h3: data = 14'h07A5; //ADDLW 0x25,1    ram[25]=6
12            11'h4: data = 14'h3005; //MOVLW 5        w=5
13            11'h5: data = 14'h0725; //ADDWF 0x25,0    w=11
14            11'h6: data = 14'h3E02; //ADDLW 2        w=13
15            11'h7: data = 14'h05A5; //ANDWF 0x25,1    ram[25]=4
16            11'h8: data = 14'h03A5; //DECF 0x25      ram[25]=3
17            11'h9: data = 14'h09A5; //COMF 0x25     ram[25]=252
18            11'ha: data = 14'h280A; //GOTO 8
19            //MPLAB清除暫存器的指令
20            11'hb: data = 14'h3400;
21            11'hc: data = 14'h3400;
22            default: data = 14'h0;
23        endcase
24    end
25    assign Rom_data_out = data;
26
27 endmodule
```

```

1 module single_port_ram_128x8(
2     input [7:0]data,
3     input [6:0]addr,
4     input ram_en,
5     input clk,
6     output logic [7:0] ram_out
7 );
8     // Declare the RAM variable
9     //reg [DATA_WIDTH-1:0] ram[2**ADDR_WIDTH-1:0];
10    logic [7:0] ram[127:0];
11
12    always_ff @(posedge clk)
13    begin
14        // Write
15        if (ram_en)
16            ram[addr] <= data;
17    end
18
19    // Continuous assignment implies read returns NEW data.
20    // This is the natural behavior of the TriMatrix memory
21    // blocks in Single Port mode.
22
23    assign ram_out = ram[addr];
24 endmodule
25
26

```

```

1 module ALU (
2     input [3:0] op,
3     input [7:0] w_q, mux1_out,
4     output logic [7:0] alu_q
5 );
6     always_comb
7     begin
8         case(op)
9             0: alu_q = mux1_out + w_q;
10            1: alu_q = mux1_out - w_q;
11            2: alu_q = mux1_out & w_q;
12            3: alu_q = mux1_out | w_q;
13            4: alu_q = mux1_out ^ w_q; //XOR
14            5: alu_q = mux1_out;
15            6: alu_q = mux1_out + 1;
16            7: alu_q = mux1_out - 1;
17            8: alu_q = 0;
18            9: alu_q = ~mux1_out;
19            default: alu_q = mux1_out + w_q;
20        endcase
21    end
22
23 endmodule

```

```

1  module cpu (
2      input clk,
3      input reset,
4      //output logic [13:0] IR
5      output logic [7:0] w_q
6  );
7      logic [13:0] rom_q, ir_q;
8      logic [10:0] pc_next, pc_q, mar_q;
9      logic load_pc, load_mar, load_ir, reset_ir, load_w, sel_pc, ram_en, sel_alu, d;
10     logic [3:0] ps,ns;
11     //logic [7:0] w_q
12     logic [7:0] alu_q, ram_out, mux1_out;
13     logic [3:0] op;
14     logic [5:0] opcode;
15     //mux 0
16     always_comb begin
17         if(sel_pc) begin
18             pc_next = ir_q;
19         end
20         else begin
21             pc_next = pc_q + 1;
22         end
23     end
24
25     //pc
26     always_ff @( posedge clk ) begin
27         if(reset)
28             pc_q <= 0;
29         else if(load_pc)
30             pc_q <= pc_next;
31     end
32
33     //mar
34     always_ff @( posedge clk ) begin
35         if(load_mar)
36             mar_q <= pc_q;
37     end
38
39     //ROM
40     Program_Rom ROM_1(
41         .Rom_addr_in(mar_q),
42         .Rom_data_out(rom_q)
43     );
44
45     //IR
46     always_ff @( posedge clk ) begin
47         if(reset)
48             ir_q <= 0;
49         else if(load_ir)
50             ir_q <= rom_q;

```

```

51     end
52
53     //RAM
54     single_port_ram_128x8 single_port_ram_128x8_1(
55         .data(alu_q),
56         .addr(ir_q[6:0]),
57         .ram_en(ram_en),
58         .clk(clk),
59         .ram_out(ram_out)
60     );
61
62     //mux 1
63     always_comb begin
64         if(sel_alu) begin
65             mux1_out = ram_out;
66         end
67         else begin
68             mux1_out = ir_q;
69         end
70     end
71
72     assign d = ir_q[7];
73     assign MOVLW = (ir_q[13:8]==6'h30);
74     assign ADDLW = (ir_q[13:8]==6'h3E);
75     assign IORLW = (ir_q[13:8]==6'h38);
76     assign ANDLW = (ir_q[13:8]==6'h39);
77     assign SUBLW = (ir_q[13:8]==6'h3C);
78     assign XORLW = (ir_q[13:8]==6'h3A);
79
80     assign ADDWF = (ir_q[13:8]==6'h07);
81     assign ANDWF = (ir_q[13:8]==6'h05);
82     assign CLRF = (ir_q[13:8]==6'h01 && d==1);
83     assign CLRW = (ir_q[13:4]==10'h010 && ir_q[3:2]==2'h0);
84     assign COMF = (ir_q[13:8]==6'h09);
85     assign DECF = (ir_q[13:8]==6'h03);
86     assign GOTO = (ir_q[13:11]==3'b101);
87
88     //ALU
89     ALU ALU_1(
90         .op(op),
91         .w_q(w_q),
92         .mux1_out(mux1_out),
93         .alu_q(alu_q)
94     );
95
96     //register
97     always_ff @( posedge clk ) begin
98         if(load_w)
99             w_q <= alu_q;
100     end

```

```
101
102 //controller
103 parameter T0 = 0;
104 parameter T1 = 1;
105 parameter T2 = 2;
106 parameter T3 = 3;
107 parameter T4 = 4;
108 parameter T5 = 5;
109 parameter T6 = 6;
110
111 always_ff @( posedge clk ) begin
112     if(reset) ps <= 0;
113     else ps <= ns;
114 end
115
116 always_comb begin
117     sel_alu = 0;
118     sel_pc = 0;
119     load_mar = 0;
120     load_pc = 0;
121     reset_ir = 1;////////////////////////////////////
122     load_ir = 0;
123     load_w = 0;
124     ram_en=0;
125     op =0;
126     ns=0;
127     case(ps)
128         T0: begin
129             ns = T1;
130         end
131         T1: begin
132             load_mar = 1;
133             load_pc = 0;
134             reset_ir = 0;
135             load_ir = 0;
136             load_w = 0;
137             ns = T2;
138         end
139         T2: begin
140             sel_pc = 0;
141             load_mar = 0;
142             load_pc = 1;
143             reset_ir = 0;
144             load_ir = 0;
145             load_w = 0;
146             ns = T3;
147         end
148         T3: begin
149             load_mar = 0;
150             load_pc = 0;
```

```
151         reset_ir = 0;
152         load_ir = 1;
153         load_w = 0;
154         ns = T4;
155     end
156     T4: begin
157         load_mar = 0;
158         load_pc = 0;
159         reset_ir = 0;
160         load_ir = 0;
161
162         if(MOVLW) begin
163             sel_alu = 0;
164             op = 5;
165             load_w = 1;
166         end
167         else if(ADDLW) begin
168             sel_alu = 0;
169             op = 0;
170             load_w = 1;
171         end
172         else if(IORLW) begin
173             sel_alu = 0;
174             op = 3;
175             load_w = 1;
176         end
177         else if(ANDLW) begin
178             sel_alu = 0;
179             op = 2;
180             load_w = 1;
181         end
182         else if(SUBLW) begin
183             sel_alu = 0;
184             op = 1;
185             load_w = 1;
186         end
187         else if(XORLW) begin
188             sel_alu = 0;
189             op = 4;
190             load_w = 1;
191         end
192
193
194         else if(GOTO) begin
195             sel_pc = 1;
196             load_pc = 1;
197         end
198         else if(ADDWF) begin
199             op = 0;
200             sel_alu = 1;
```



```

201         if(d) begin
202             ram_en = 1;
203         end
204         else begin
205             load_w = 1;
206         end
207     end
208     else if(ANDWF) begin
209         op = 2;
210         sel_alu = 1;
211         if(d) begin
212             ram_en = 1;
213         end
214         else begin
215             load_w = 1;
216         end
217     end
218     else if(CLRF) begin
219         op = 8;
220         ram_en = 1;
221     end
222     else if(CLRW) begin
223         op = 8;
224         load_w = 1;
225     end
226     else if(COMF) begin
227         op = 9;
228         sel_alu = 1;
229         ram_en = 1;
230     end
231     else if(DECF) begin
232         op = 7;
233         sel_alu = 1;
234         ram_en = 1;
235     end
236     ns = T5;
237 end
238 T5: begin
239     ns = T6;
240 end
241 T6: begin
242     ns = T1;
243 end
244 endcase
245 end
246 endmodule

```

```

1 module testbench;
2
3     logic clk,reset;
4     logic [7:0] w_q;
5
6     cpu cpu_test(
7         .clk(clk),
8         .reset(reset),
9         .w_q(w_q)
10    );
11
12    always #10 clk = ~clk;
13    initial begin
14        clk = 0; reset = 1;
15        #20 reset = 0;
16        #1300 $stop;
17    end
18 endmodule


```

```

1 onerror {resume}
2 quietly WaveActivateNextPane {} 0
3
4 add wave -noupdate -divider {1114}
5
6 add wave -noupdate -format Literal -radix decimal /testbench/cpu_test/clk
7 add wave -noupdate -format Literal -radix decimal /testbench/cpu_test/reset
8 add wave -noupdate -format Literal -radix decimal /testbench/cpu_test/w_q
9 add wave -noupdate -format Literal -radix Unsigned /testbench/cpu_test/ram_out

```

● 模擬結果與結果說明：

 

一開始 清空 ram[25]和 w，接下來把 w 設成 6.....

● 結論與心得：

本周的教學內容和作業又更上一層樓，上週只是從指令裡面去做運算，本周又增加了暫存器，逐漸越來越像一個 CPU 的樣子。除此之外，老師也把期中考的成績加 5 分，非常謝謝老師，也謝謝助教在期中考時在最後一刻讓我 demo，成功過關。