

注意

1. 繳交時一律轉 PDF 檔
2. 一人繳交一份
3. 檔名：學號_HW?.pdf
檔名請按照作業檔名格式進行填寫
未依照格式不予批改

2022/12/5

實驗十一

暫存器定址指令

姓名：張銀軒 學號：00957050

班級：資工 3A

E-mail：00957050@mail.ntou.edu.tw

2022/12/5

● 實驗說明：

1. 如圖所示，設計一個架構實現條件跳躍指令
2. 輸入：clk, reset
3. 輸出：w_q[7:0]

請務必按照規定的 input 及 output 來做


請建一個 MPLAB 專案，打入下方給的組合語言 code，BUILD 並生成 HEX 檔，再將 HEX 轉成 Program_Rom，模擬結果請參考下方的圖

```
#include <pl6Lf1826.inc> ; Include file locat
;

temp equ 0x25
;*****
; Program start *
;*****
org 0x00 ; reset vector

clrf temp ; //ram[37]<=0
clrw ; //w<=0
movlw 28 ; //w<=0x28
movwf temp ; //ram[37]<=0x28
asrf temp,1 ; //ram[37]<=0x14
rlf temp,0 ; //w<=0x28
lsrf temp,1 ; //ram[37]<=0x0a
lslf temp,0 ; //w<=0x14
rrf temp,1 ; //ram[37]<=0x05
swapf temp,0 ; //w<=0x50
goto $
end
```

組合語言

 

模擬結果

● 系統架構程式碼、測試資料程式碼與程式碼說明

截圖請善用 win+shift+S

```

1 module Program_Rom(
2     output logic [13:0] Rom_data_out,
3     input [10:0] Rom_addr_in
4 );
5
6     logic [13:0] data;
7     always_comb
8     begin
9         case (Rom_addr_in)
10             10'h0 : data = 14'h01A5;
11             10'h1 : data = 14'h0103;
12             10'h2 : data = 14'h3028;
13             10'h3 : data = 14'h00A5;
14             10'h4 : data = 14'h37A5;
15             10'h5 : data = 14'h0D25;
16             10'h6 : data = 14'h36A5;
17             10'h7 : data = 14'h3525;
18             10'h8 : data = 14'h0CA5;
19             10'h9 : data = 14'h0E25;
20             10'ha : data = 14'h280A;
21             10'hb : data = 14'h3400;
22             10'hc : data = 14'h3400;
23             default: data = 14'h0;
24         endcase
25     end
26
27     assign Rom_data_out = data;
28
29 endmodule
30

```

```

1 module single_port_ram_128x8(
2     input [7:0]data,
3     input [6:0]addr,
4     input ram_en,
5     input clk,
6     output logic [7:0] ram_out
7 );
8     // Declare the RAM variable
9     //reg [DATA_WIDTH-1:0] ram[2**ADDR_WIDTH-1:0];
10    logic [7:0] ram[127:0];
11
12    always_ff @(posedge clk)
13    begin
14        // Write
15        if (ram_en)
16            ram[addr] <= data;
17    end
18
19    // Continuous assignment implies read returns NEW data.
20    // This is the natural behavior of the TriMatrix memory
21    // blocks in Single Port mode.
22
23    assign ram_out = ram[addr];
24 endmodule
25
26

```

```

1 module ALU (
2     input [3:0] op,
3     input [7:0] w_q, mux1_out,
4     output logic [7:0] alu_q
5 );
6 always_comb
7 begin
8     case(op)
9         4'h0: alu_q = mux1_out[7:0] + w_q;
10        4'h1: alu_q = mux1_out[7:0] - w_q;
11        4'h2: alu_q = mux1_out[7:0] & w_q;
12        4'h3: alu_q = mux1_out[7:0] | w_q;
13        4'h4: alu_q = mux1_out[7:0] ^ w_q; //XOR
14        4'h5: alu_q = mux1_out[7:0];
15        4'h6: alu_q = mux1_out[7:0] + 1;
16        4'h7: alu_q = mux1_out[7:0] - 1;
17        4'h8: alu_q = 0;
18        4'h9: alu_q = ~mux1_out[7:0];
19        4'ha: alu_q = { mux1_out[7],mux1_out[7:1] }; //ASRF arithmetic right shift
20        4'hB: alu_q = { mux1_out[6:0], 1'b0 }; //LSLF logical left shift
21        4'hC: alu_q = { 1'b0, mux1_out[7:1] }; //LSRF logical right shift
22        4'hD: alu_q = { mux1_out[6:0], mux1_out[7] }; //RLF rotate left f
23        4'hE: alu_q = { mux1_out[0], mux1_out[7:1] }; //RRF rotate right f
24        4'hF: alu_q = { mux1_out[3:0], mux1_out[7:4] }; //{m7, m6,...m4, m3,...m0} => {m3,...m0, m7, m6,...m4}
25        default: alu_q = mux1_out[7:0] + w_q;
26    endcase
27 end
28
29 endmodule

```

```

1 module cpu (
2     input clk,
3     input reset,
4     output logic [7:0] port_b_out
5 );
6     logic [13:0] rom_q, ir_q;
7     logic [10:0] pc_next, pc_q, mar_q;
8     logic load_pc, load_mar, load_ir, reset_ir, load_w, sel_pc, ram_en, sel_alu, d, sel_bus;
9     logic load_port_b;
10    logic [3:0] ps,ns;
11    logic [7:0] w_q, alu_q, ram_out, mux1_out, bcf_mux, bsf_mux, ram_mux;
12    logic [7:0] databus;
13    logic [3:0] op;
14    logic [5:0] opcode;
15    logic [2:0] sel_bit;
16    logic [1:0] sel_ram_mux;
17    //mux 0 (select next PC address)
18    always_comb begin
19        if(sel_pc) begin
20            pc_next = ir_q;
21        end
22        else begin
23            pc_next = pc_q + 1;
24        end
25    end
26
27    //pc
28    always_ff @( posedge clk ) begin
29        if(reset)
30            pc_q <= 0;
31        else if(load_pc)
32            pc_q <= pc_next;
33    end
34
35    //mar
36    always_ff @( posedge clk ) begin
37        if(load_mar)
38            mar_q <= pc_q;
39    end
40
41    //ROM
42    Program_Rom ROM_1(
43        .Rom_addr_in(mar_q),
44        .Rom_data_out(rom_q)
45    );
46
47    //IR
48    always_ff @( posedge clk ) begin
49        if(reset)
50            ir_q <= 0;

```

```

51     else if(load_ir)
52         ir_q <= rom_q;
53     end
54
55     //RAM
56     single_port_ram_128x8 single_port_ram_128x8_1(
57         .data(databus),
58         .addr(ir_q[6:0]),
59         .ram_en(ram_en),
60         .clk(clk),
61         .ram_out(ram_out)
62     );
63
64     assign sel_bit = ir_q[9:7];
65
66     //BCF mux
67     always_comb begin
68         case (sel_bit)
69             3'b000: bcf_mux = ram_out & 8'b1111_1110;
70             3'b001: bcf_mux = ram_out & 8'b1111_1101;
71             3'b010: bcf_mux = ram_out & 8'b1111_1011;
72             3'b011: bcf_mux = ram_out & 8'b1111_0111;
73             3'b100: bcf_mux = ram_out & 8'b1110_1111;
74             3'b101: bcf_mux = ram_out & 8'b1101_1111;
75             3'b110: bcf_mux = ram_out & 8'b1011_1111;
76             3'b111: bcf_mux = ram_out & 8'b0111_1111;
77         endcase
78     end
79
80     //BSF mux
81     always_comb begin
82         case (sel_bit)
83             3'b000: bsf_mux = ram_out | 8'b0000_0001;
84             3'b001: bsf_mux = ram_out | 8'b0000_0010;
85             3'b010: bsf_mux = ram_out | 8'b0000_0100;
86             3'b011: bsf_mux = ram_out | 8'b0000_1000;
87             3'b100: bsf_mux = ram_out | 8'b0001_0000;
88             3'b101: bsf_mux = ram_out | 8'b0010_0000;
89             3'b110: bsf_mux = ram_out | 8'b0100_0000;
90             3'b111: bsf_mux = ram_out | 8'b1000_0000;
91         endcase
92     end
93
94     //ram mux (select data into mux1)
95     always_comb begin
96         case (sel_ram_mux)
97             0: ram_mux = ram_out;
98             1: ram_mux = bcf_mux;
99             2: ram_mux = bsf_mux;
100        endcase

```

```

101     end
102
103     //mux 1 (select data into ALU)
104     always_comb begin
105         if(sel_alu) begin
106             mux1_out = ram_mux;
107         end
108         else begin
109             mux1_out = ir_q;
110         end
111     end
112
113     assign d = ir_q[7];
114     assign MOVLW = (ir_q[13:8]==6'h30);
115     assign ADDLW = (ir_q[13:8]==6'h3E);
116     assign IORLW = (ir_q[13:8]==6'h38);
117     assign ANDLW = (ir_q[13:8]==6'h39);
118     assign SUBLW = (ir_q[13:8]==6'h3C);
119     assign XORLW = (ir_q[13:8]==6'h3A);
120
121     assign ADDWF = (ir_q[13:8]==6'h07);
122     assign ANDWF = (ir_q[13:8]==6'h05);
123     assign CLRF = (ir_q[13:8]==6'h01 && d==1);
124     assign CLRW = (ir_q[13:4]==10'h010 && ir_q[3:2]==2'h0);
125     assign COMF = (ir_q[13:8]==6'h09);
126     assign DECF = (ir_q[13:8]==6'h03);
127     assign GOTO = (ir_q[13:11]==3'b101);
128
129     assign INCF = (ir_q[13:8]==6'h0A);
130     assign IORWF = (ir_q[13:8]==6'h04);
131     assign MOVF = (ir_q[13:8]==6'h08);
132     assign MOVWF = (ir_q[13:8]==6'h00 && ir_q[7]==1'b1);
133     assign SUBWF = (ir_q[13:8]==6'h02);
134     assign XORWF = (ir_q[13:8]==6'h06);
135
136     assign BCF = (ir_q[13:12]==2'b01 && ir_q[11:10]==2'b00);
137     assign BSF = (ir_q[13:12]==2'b01 && ir_q[11:10]==2'b01);
138     assign BTFSC = (ir_q[13:12]==2'b01 && ir_q[11:10]==2'b10);
139     assign BTFSS = (ir_q[13:12]==2'b01 && ir_q[11:10]==2'b11);
140     assign DECFSZ = (ir_q[13:8]==6'h0B);
141     assign INCFSZ = (ir_q[13:8]==6'h0F);
142
143     assign btfsc_skip_bit = (ram_out[ir_q[9:7]]==0);
144     assign btfss_skip_bit = (ram_out[ir_q[9:7]]==1);
145     assign btfsc_btfss_skip_bit = (BTFSC&btfsc_skip_bit) |
146                                     (BTFSS&btfss_skip_bit);
147     assign ASRF = (ir_q[13:8]==6'h37);
148     assign LSLF = (ir_q[13:8]==6'h35);
149     assign LSRF = (ir_q[13:8]==6'h36);
150     assign RLF = (ir_q[13:8]==6'h0D);

```

```

151     assign    RRF = (ir_q[13:8]==6'h0C);
152     assign    SWAP = (ir_q[13:8]==6'h0E); //{m7, m6,...m4, m3,...m0} => {m3,...m0, m7, m6,...m4}
153     //ALU
154     ALU ALU_1(
155         .op(op),
156         .w_q(w_q),
157         .mux1_out(mux1_out),
158         .alu_q(alu_q)
159     );
160     assign aluout_zero = (alu_q == 0);
161
162     //register
163     always_ff @( posedge clk ) begin
164         if(load_w)
165             w_q <= alu_q;
166     end
167
168     //mux 2 (select data into RAM)
169     always_comb begin
170         if(sel_bus) begin
171             databus = w_q;
172         end
173         else begin
174             databus = alu_q;
175         end
176     end
177
178     //Port_b
179     always_ff @( posedge clk ) begin
180         if(reset) begin
181             port_b_out <= 0;
182         end
183         else if(load_port_b) begin
184             port_b_out <= databus;
185         end
186     end
187
188     assign addr_port_b = (ir_q[6:0] == 7'h0D);
189
190     //controller
191     parameter T0 = 0;
192     parameter T1 = 1;
193     parameter T2 = 2;
194     parameter T3 = 3;
195     parameter T4 = 4;
196     parameter T5 = 5;
197     parameter T6 = 6;
198
199     always_ff @( posedge clk ) begin
200         if(reset) ps <= 0;

```

```

201     else ps <= ns;
202 end
203
204 always_comb begin
205     sel_alu = 0;
206     sel_pc = 0;
207     load_mar = 0;
208     load_pc = 0;
209     reset_ir = 1;
210     load_ir = 0;
211     load_w = 0;
212     ram_en = 0;
213     op = 0;
214     sel_ram_mux = 0;
215     sel_bus = 0;
216     load_port_b = 0;
217     ns = 0;
218     case(ps)
219         T0: begin
220             ns = T1;
221         end
222         T1: begin
223             load_mar = 1;
224             load_pc = 0;
225             reset_ir = 0;
226             load_ir = 0;
227             load_w = 0;
228             ns = T2;
229         end
230         T2: begin
231             sel_pc = 0;
232             load_mar = 0;
233             load_pc = 1;
234             reset_ir = 0;
235             load_ir = 0;
236             load_w = 0;
237             ns = T3;
238         end
239         T3: begin
240             load_mar = 0;
241             load_pc = 0;
242             reset_ir = 0;
243             load_ir = 1;
244             load_w = 0;
245             ns = T4;
246         end
247         T4: begin
248             load_mar = 0;
249             load_pc = 0;
250             reset_ir = 0;

```



```
251         load_ir = 0;
252
253         if(MOVLW) begin
254             sel_alu = 0;
255             op = 5;
256             load_w = 1;
257         end
258         else if(ADDLW) begin
259             sel_alu = 0;
260             op = 0;
261             load_w = 1;
262         end
263         else if(IORLW) begin
264             sel_alu = 0;
265             op = 3;
266             load_w = 1;
267         end
268         else if(ANDLW) begin
269             sel_alu = 0;
270             op = 2;
271             load_w = 1;
272         end
273         else if(SUBLW) begin
274             sel_alu = 0;
275             op = 1;
276             load_w = 1;
277         end
278         else if(XORLW) begin
279             sel_alu = 0;
280             op = 4;
281             load_w = 1;
282         end
283
284
285         else if(GOTO) begin
286             sel_pc = 1;
287             load_pc = 1;
288         end
289         else if(ADDWF) begin
290             op = 0;
291             sel_alu = 1;
292             if(d) begin
293                 ram_en = 1;
294             end
295             else begin
296                 load_w = 1;
297             end
298         end
299         else if(ANDWF) begin
300             op = 2;
```

```
301         sel_alu = 1;
302         if(d) begin
303             ram_en = 1;
304         end
305         else begin
306             load_w = 1;
307         end
308     end
309     else if(CLRF) begin
310         op = 8;
311         ram_en = 1;
312     end
313     else if(CLRW) begin
314         op = 8;
315         load_w = 1;
316     end
317     else if(COMF) begin
318         op = 9;
319         sel_alu = 1;
320         ram_en = 1;
321     end
322     else if(DECf) begin
323         op = 7;
324         sel_alu = 1;
325         ram_en = 1;
326     end
327
328     else if(INCF) begin
329         op = 6;
330         sel_alu = 1;
331         if(d) begin
332             ram_en = 1;
333             sel_bus = 0;
```

```
334         end
335         else begin
336             load_w = 1;
337         end
338     end
339     else if(IORWF) begin
340         op = 3;
341         sel_alu = 1;
342         if(d) begin
343             ram_en = 1;
344             sel_bus = 0;
345         end
346         else begin
347             load_w = 1;
348         end
349     end
350     else if(MOVF) begin
351         op = 5;
352         sel_alu = 1;
353         if(d) begin
354             ram_en = 1;
355             sel_bus = 0;
356         end
357         else begin
358             load_w = 1;
359         end
360     end
361     else if(MOVWF) begin
362         sel_bus = 1;
363         if(addr_port_b)begin
364             load_port_b = 1;
365         end
366         else begin
```

```
367         ram_en = 1;
368     end
369 end
370 else if(SUBWF) begin
371     op = 1;
372     sel_alu = 1;
373     if(d) begin
374         ram_en = 1;
375         sel_bus = 0;
376     end
377     else begin
378         load_w = 1;
379     end
380 end
381 else if(XORWF) begin
382     op = 4;
383     sel_alu = 1;
384     if(d) begin
385         ram_en = 1;
386         sel_bus = 0;
387     end
388     else begin
389         load_w = 1;
390     end
391 end
392 else if(BCF)begin
393     sel_alu = 1;
394     sel_ram_mux = 1;
395     op = 5;
396     sel_bus = 0;
397     ram_en = 1;
398 end
399 else if(BSF)begin
400     sel_alu = 1;
```

```
401         sel_ram_mux = 2;
402         op = 5;
403         sel_bus = 0;
404         ram_en = 1;
405     end
406     else if(BTFSC || BTFSS)begin
407         if( btfsc_btfss_skip_bit )begin
408             load_pc = 1;
409             sel_pc = 0;
410         end
411     end
412     else if(DECFSZ)begin
413         sel_alu = 1;
414         op = 7;
415         if(aluout_zero)begin
416             load_pc = 1;
417             sel_pc = 0;
418         end
419
420         if(d)begin
421             ram_en = 1;
422             sel_bus = 0;
423         end
424         else begin
425             load_w = 1;
426         end
427     end
428     else if(INCFSZ) begin
429         sel_alu = 1;
430         op = 6;
431         if(aluout_zero)begin
432             load_pc = 1;
433             sel_pc = 0;
```

```
434         end
435
436         if(d)begin
437             ram_en = 1;
438             sel_bus = 0;
439         end
440         else begin
441             load_w = 1;
442         end
443     end
444
445     else if(ASRF) begin
446         sel_alu = 1;
447         sel_ram_mux = 0;
448         op = 4'hA;
449         if(d)begin
450             sel_bus = 0;
451             ram_en = 1;
452         end
453         else begin
454             load_w = 1;
455         end
456     end
457     if(LSLF) begin
458         sel_alu = 1;
459         sel_ram_mux = 0;
460         op = 4'hB;
461         if(d)begin
462             sel_bus = 0;
463             ram_en = 1;
464         end
465         else begin
466             load_w = 1;
```

```
467         end
468     end
469     if(LSRF) begin
470         sel_alu = 1;
471         sel_ram_mux = 0;
472         op = 4'hC;
473         if(d)begin
474             sel_bus = 0;
475             ram_en = 1;
476         end
477         else begin
478             load_w = 1;
479         end
480     end
481     if(RLF) begin
482         sel_alu = 1;
483         sel_ram_mux = 0;
484         op = 4'hD;
485         if(d)begin
486             sel_bus = 0;
487             ram_en = 1;
488         end
489         else begin
490             load_w = 1;
491         end
492     end
493     if(RRF) begin
494         sel_alu = 1;
495         sel_ram_mux = 0;
496         op = 4'hE;
497         if(d)begin
498             sel_bus = 0;
499             ram_en = 1;
500         end
501     end
```

```

501         else begin
502             load_w = 1;
503         end
504     end
505     if(SWAP) begin
506         sel_alu = 1;
507         sel_ram_mux = 0;
508         op = 4'hF;
509         if(d)begin
510             sel_bus = 0;
511             ram_en = 1;
512         end
513     else begin
514         load_w = 1;
515     end
516 end
517 ns = T5;
518 end
519 T5: begin
520     ns = T6;
521 end
522 T6: begin
523     ns = T1;
524 end
525 endcase
526 end
527 endmodule

```

```

1 module testbench;
2
3     logic clk,reset;
4     logic [7:0] port_b_out;
5
6     cpu cpu_test(
7         .clk(clk),
8         .reset(reset),
9         .port_b_out(port_b_out)
10    );
11
12    always #10 clk = ~clk;
13    initial begin
14        clk = 0; reset = 1;
15        #20 reset = 0;
16        #9000 $stop;
17    end
18 endmodule


```

```

1 onerror {resume}
2 quietly WaveActivateNextPane {} 0
3
4 add wave -noupdate -divider {1205}
5
6 add wave -noupdate -format Literal -radix decimal      /testbench/cpu_test/clk
7 add wave -noupdate -format Literal -radix decimal      /testbench/cpu_test/reset
8 add wave -noupdate -format Literal -radix Hexadecimal  /testbench/cpu_test/w_q
9 add wave -noupdate -format Literal -radix Hexadecimal  /testbench/cpu_test/single_port_ram_128x8_1/ram\[37\]

```

● 模擬結果與結果說明：

 

能夠依照 Program_Rom 的指令，做出正確的模擬(3028=>MOVLW 28, 如上圖所示 w=28...)

● 結論與心得：

今天又增加了一些位移的指令，與此同時 ALU 也進行了擴充，有了前幾週的經驗，今天很快就找到自己的一個錯誤，但是還剩下一個錯誤，後來經過助教指導，才知道我的邏輯沒有寫錯，只是 wave 檔選擇的線有誤，修正過後就是正確的波形圖，十分感謝助教的指導，今天的錯誤我會謹記在心。